

Course Title:	Digital Systems Engineering
Course Number:	COE758
Semester/Year (e.g.F2016)	F2023

Instructor:	Dr. Geurkov
--------------------	-------------

<i>Assignment/Lab Number:</i>	Cache Controller
<i>Assignment/Lab Title:</i>	Design Project 1

<i>Submission Date:</i>	2023-10-21
<i>Due Date:</i>	2023-10-25

Student LAST Name	Student FIRST Name	Student Number	Section	Signature*
Zelenovic	Danilo	501032542	11	DZ

*By signing above you attest that you have contributed to this written lab report and confirm that all work you have contributed to this lab report is your own work. Any suspicion of copying or plagiarism in this work will result in an investigation of Academic Misconduct and may result in a "0" on the work, an "F" in the course, or possibly more severe penalties, as well as a Disciplinary Notice on your academic record under the Student Code of Academic Conduct, which can be found online at: <http://www.ryerson.ca/senate/current/pol60.pdf>

Abstract

The goal of this design project is to design and create an SDRAM controller as well as a cache memory system, using a cache controller and an SRAM cache. The CPU is to issue 16-bit address words (may be less if not possible), to the cache controller, and it is to act accordingly. The cache controller must be capable of performing 4 cases:

1. Write a word to the cache (hit)
2. Read a word from the cache (hit)
3. Read or write from or to the cache (miss) with the dirty bit set to 0
4. Read or write from or to the cache (miss) with the dirty bit set as 1

The proper functionality can be tested with the simulated waveforms in order to ensure the project is functional.

Introduction

In nearly all modern computers, there are multiple different memories, all of which have a purpose of storing, reading, and processing data and information, however, each level has a different purpose or usage within the system. As an example, RAM provides very fast read/write but this memory is lost or reset when the system is turned off. ROM is also a form of memory; however, it is non-volatile and stores read-only data which is permanently stored. Withing RAM, there are many categories such as SRAM (static RAM), DRAM (dynamic RAM), SDRAM (synchronized DRAM), and more. These memories, as well as others such as main memory, secondary storage are placed into a memory hierarchy. As a general rule, the closer the memory is to the CPU, the faster the access speed, but smaller the size of available storage, and more expensive it is.

System Specifications

There are 4 behavioral cases we must implemented in the cache controller, these being:

1. When the cache controller receives a request to write from the CPU, a cache hit is detected. In this situation, the index and offset data provided by the CPU is then moved over to the SRAM as the address where the data will be written. Next, the multiplexer writes data to the SRAM received from the CPU only if/when the write bit is enabled, otherwise it is not able to do so.

Figure 1: CPU Symbol

Cache Controller:

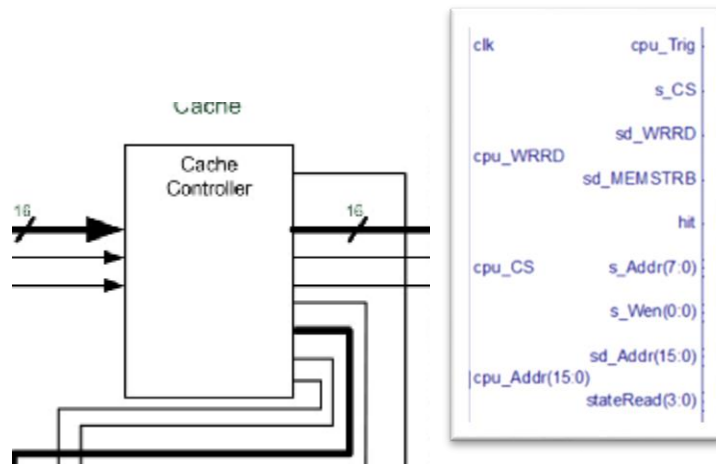


Figure 2: Cache controller symbol

SDRAM Controller:

 


Figure 3: SDRAM controller symbol

Cache SRAM:

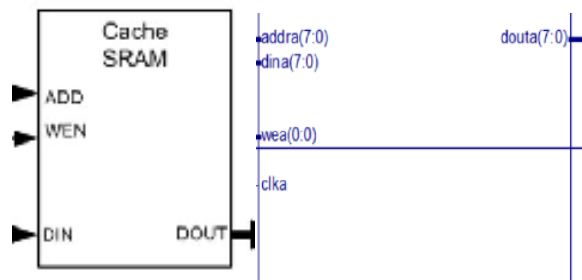


Figure 4: Cache SRAM symbol

2-to-1 Multiplexer:

 


Figure 5: 2-to-1 multiplexer symbol

1-to-2 Demultiplexer:

 


Figure 6: 1-to-2 demultiplexer symbol

The **figures** above (1-6) illustrate the individual components used in the block diagram used to create the entire cache controller. Each symbol was created by stating components in each file. After each component was verified, the block was created using “create schematic symbol”. After this part, we opened a schematic file to link each symbol together with wiring between the appropriate inputs and outputs. This can be seen in the block diagram **Figure 7 and 8**.

b. Block diagrams

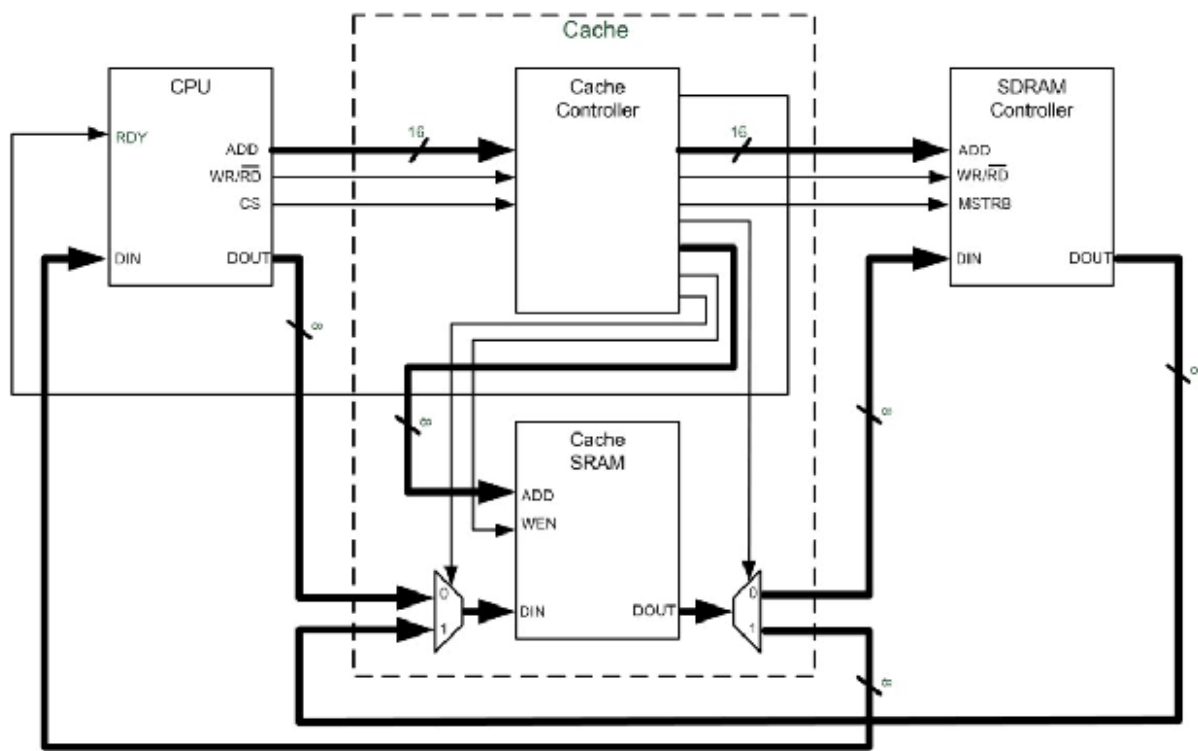


Figure 7: Complete cache system

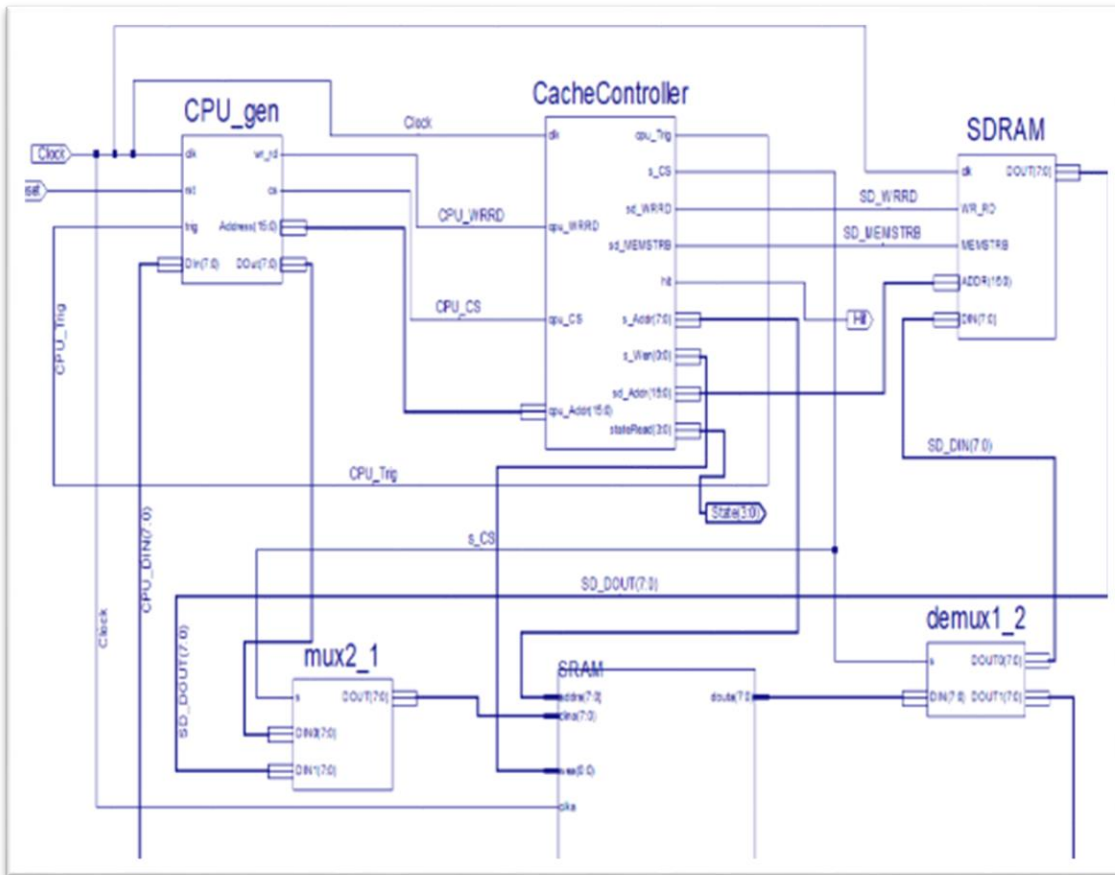


Figure 8: Block Diagram

Figure 8 shows the full block diagram of connections for the cache controller with each component wired, as per the manual instructions shown in **Figure 7**. The thin wires have only 1 bit connection, while thicker wires represent multiple bits to be transmitted. The main inputs are clock and reset. Clock signal is used to synchronize the CPU, cache controller, SDRAM and SRAM. The CPU transmits an address to cache controller. The cache controller then must read or write to SRAM, which depends on statuses in cache controller. Along with this process, the CPU will also transmit an address to the SRAM using the 2-to-1 multiplexer with the selector bit coming from the cache controller itself. The multiplexer and demultiplexer are used to transmit data to CPU, data from the SRAM and comparing values in order to determine whether a cache hit or miss has occurred. The SRAM which is connected to the (de)multiplexers is the cache's memory component which stores data. This component receives signals from all other components. The SDRAM's job is to evaluate data transmitted by the cache controller and also taking input from the clock and demultiplexer.

c. State diagrams

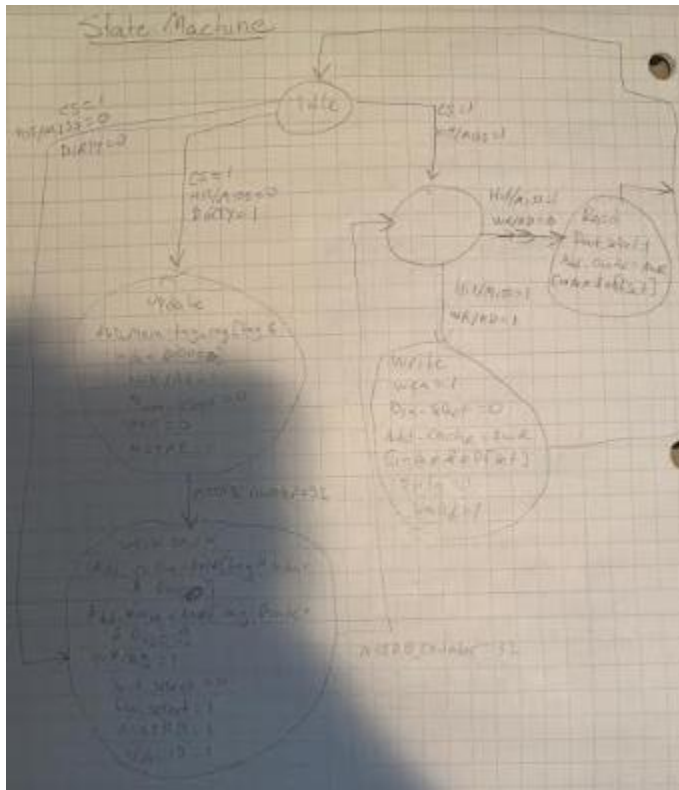


Figure 9: State diagram

The figure above indicated a finite state machine (FSM) used by our cache controller. First, the controller must fetch an address from the CPU. The CPU then issues the read/write enable bits as well as the control signals required such as addresses to be fetched by the cache controller. Then, the cache controller will search the SRAM and see if there is data in that specified location (hit) or if there is not any (miss). If a hit is detected by the cache controller, it will then begin to read/write the data from SRAM and send that information to the CPU. Afterwards, the signal will be switched to indicate that the cache controller is in an idle state, and it is awaiting further instructions from the CPU. Once it receives instructions, it will return to the first state of checking whether this value is in the cache or not. If a miss is detected by the cache controller, the cache controller moves to a state that reflects this, depending on the value of the dirty bit. If the dirty bit is 1, it will enter state where it writes the block to SDRAM, then the controller will switch states to read/write to/from SRAM. However, if the miss was detected, and dirty bit is 0, the cache controller will skip the write operation and will read directly to SDRAM. Finally, it will switch states after retrieving data from SDRAM in order to store it in SRAM cache memory. It will then wait for another instruction from the CPU.

d. Process diagrams

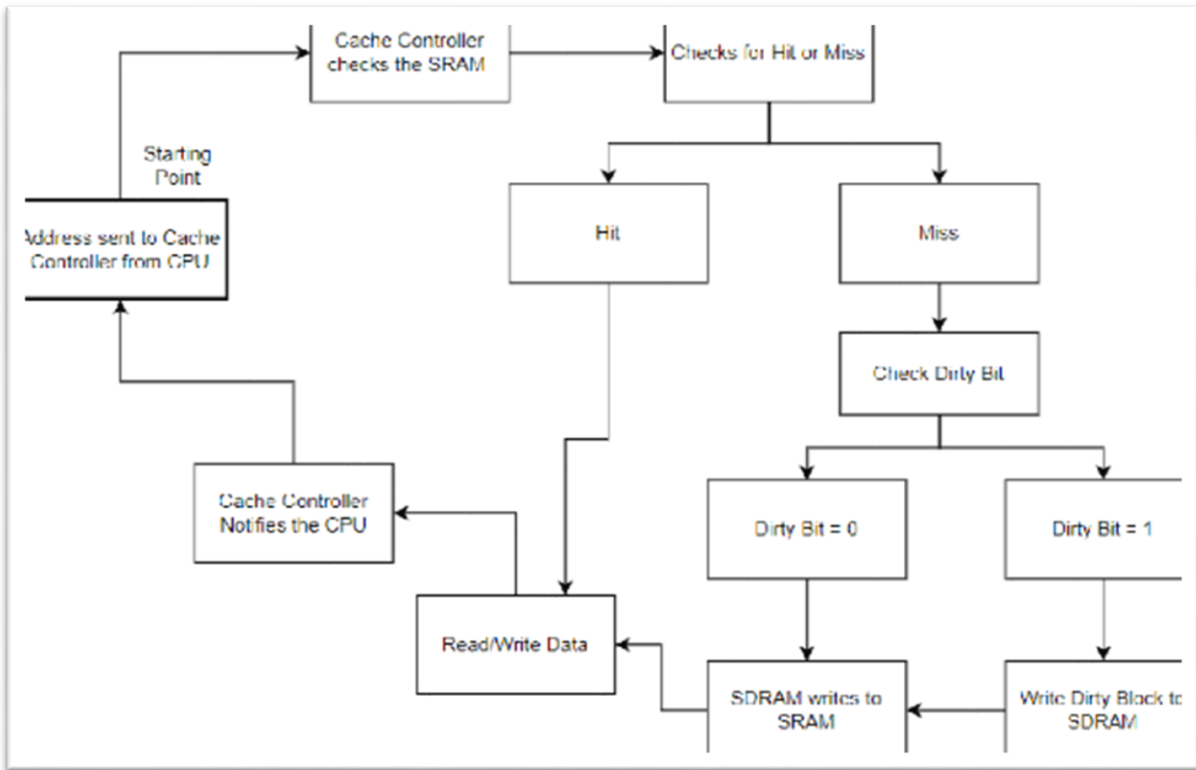


Figure 10: Process diagram

Figure 10 above illustrates the process diagram of our cache controller. The process starts when the CPU sends instructions as well as an address to the cache controller. Next, the cache controller will check the SRAM memory to determine if there is data in that location of the cache (hit or miss). If a hit is detected, the controller is able to read/write to/from the SRAM. But, if it is a miss, the controller must read the dirty bit first, in order to determine its next step. If the dirty bit is a 0, the SDRAM will write its information at that address to the SRAM and the cache controller is able to continue with the original request. The controller then lets the CPU know that it is awaiting further instructions. However, if the dirty bit is a 1, then the cache controller will copy the block back to the SDRAM before the new information is given to SRAM.

Results

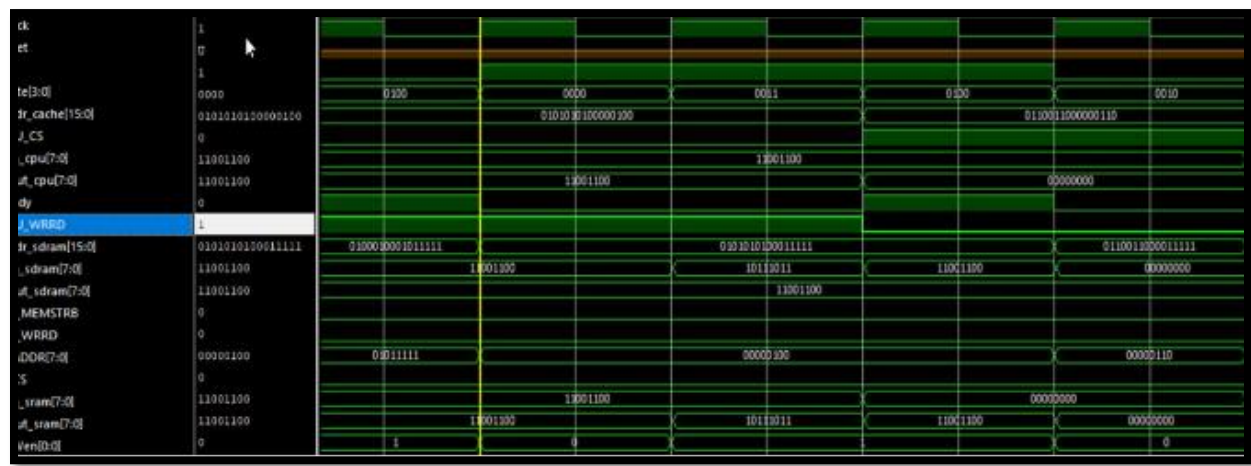


Figure 11: Functional simulation results

Figure 11 is a demonstration of the simulation depicted. At the 630 ns mark, we see the state switch, where instructions are fetched from CPU. The chip select signal is at 0 and the read/write signal is high, meaning a write operation is to be executed. Hit is a 1, meaning that a hit has been detected and a state change is done. Because of this, we see at 640 ns that Dout_SRAM is made to be same as Din_CPU, which works as required as the read operation to CPU was done properly. The controller goes back to next state and sits idly waiting for next instructions form CPU. It then repeats a similar process.

Conclusion

It appears that the cache controller designed was implemented as should be. Thanks to this project, greater knowledge, and insight into the workings of a cache controller and the cache system was developed. The importance was also showcased greatly. Why dirty bits and valid bits are used and why they increase optimization of data flow and control was also showcased during this project. This project greatly showed how memory controllers can affect time and efficiency of programs and information to be shared with other components.

Appendix/References

References:

<https://courses.torontomu.ca/d2l/le/content/792271/viewContent/5322259/View>
<https://courses.torontomu.ca/d2l/le/content/792271/viewContent/5323145/View>
<https://courses.torontomu.ca/d2l/le/content/792271/viewContent/5322257/View>
<https://courses.torontomu.ca/d2l/le/content/792271/viewContent/5322256/View>
<https://courses.torontomu.ca/d2l/le/content/792271/viewContent/5325205/View>

Sources:

```

--Library
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
entity CacheController is
  Port (
    cpu_Addr : in STD_LOGIC_VECTOR(15 downto 0);
    clk : in STD_LOGIC;
    cpu_WRRD : in STD_LOGIC;
    cpu_CS : in STD_LOGIC;
    cpu_Trig : out STD_LOGIC;

    s_Addr : out STD_LOGIC_VECTOR(7 downto 0);
    s_Wen : out STD_LOGIC_VECTOR(0 downto 0);
    s_CS : out STD_LOGIC;

    sd_Addr : out STD_LOGIC_VECTOR(15 downto 0);
    sd_WRRD : out STD_LOGIC;
    sd_MEMSTRB : out STD_LOGIC;

    stateRead : out STD_LOGIC_VECTOR(3 downto 0);
  );
end CacheController;

architecture Behavior of CacheController is
  --CPU Signals
  signal tag : STD_LOGIC_VECTOR(7 downto 0);
  signal index : STD_LOGIC_VECTOR(2 downto 0);
  signal offset : STD_LOGIC_VECTOR(4 downto 0);

  --Dirty Bit Signal
  signal dBit : STD_LOGIC_VECTOR(7 downto 0) := "00000000";

  -- Valid Bit Signal
  signal vBit : STD_LOGIC_VECTOR(7 downto 0) := "00000000";

  -- SRAM Cache Array
  type cachememory is array (7 downto 0) of STD_LOGIC_VECTOR(7 downto 0);
  signal memtag: cachememory := ((others=> (others=>'0')));

  -- SDRAM Signals
  signal counter : integer := 0;
  signal sd_Offset : integer := 0;

```

```

TYPE state_value IS (state4, state0, state1, state2, state3);
signal state_current : state_value ;
signal state : STD_LOGIC_VECTOR(3 downto 0);

begin
  process(clk, cpu_CS)
  begin
    if (clk'event AND clk = '1') then -- rising edge of clock
      State 4
      if (state_current = state4) then
        cpu_Trig <= '0';
        tag <= cpu_Addr(15 downto 8);
        index <= cpu_Addr(7 downto 5);
        offset <= cpu_Addr(4 downto 0);
        sd_Addr(15 downto 5) <= cpu_Addr(15 downto 5);
        s_Addr(7 downto 0) <= cpu_Addr(7 downto 0);
        s_Wen <= "0";
        if (vBit(to_integer(unsigned(index))) = '1' AND memtag(to_integer(unsigned(index))) = tag) then
          hit <= '1';
          state_current <= state0;
          state <= "0000";
          stateRead <= "0000";
        Cache Miss
        else
          hit <= '0';
        If Dirty Bit and Valid Bit in Block are 1
        Switches to State 2 to write back to SDRAM
        if (dBit(to_integer(unsigned(index))) = '1' AND
          vBit(to_integer(unsigned(index))) = '1') then
          state_current <= state2;
          state <= "0010";
          stateRead <= "0010";

```

```

else
    state_current <= state1;
    state <= "0001";
    stateRead <= "0001";
end if;
end if;
ate 0
elsif(state_current = state0) then
    if (cpu_WRRD = '1') then
        s_Wen <= "1";
        s_CS <= cpu_CS;
        dBit(to_integer(unsigned(index))) <= '1';
        vBit(to_integer(unsigned(index))) <= '1';
    else
        s_Wen <= "0";
        s_CS <= cpu_CS;
    end if;
    state_current <= state3;
    state <= "0011";
    stateRead <= "0011";
ate 1
elsif(state_current = state1) then
    if (counter = 64) then
        counter <= 0;
        vBit(to_integer(unsigned(index))) <= '1';
        memtag(to_integer(unsigned(index))) <= tag;
        sd_Offset <= 0;
        state_current <= state0;
        state <= "0000";
        stateRead <= "0000";
    else
        if (counter mod 2 = 1) then
            sd_MEMSTRB <= '0';
        else
            s_CS <= cpu_CS;
            sd_Addr(4 downto 0) <= STD_LOGIC_VECTOR(to_unsigned(sd_Offset, offset'length));
            sd_WRRD <= '0';
            sd_MEMSTRB <= '1';
            s_Addr(7 downto 5) <= index;
            s_Addr(4 downto 0) <=

```

```

        STD_LOGIC_VECTOR(to_unsigned(sd_Offset, offset'length));
        s_Wen <= "1";
        sd_Offset <= sd_Offset + 1;
    end if;
    counter <= counter + 1;
end if;
State 2
elsif(state_current = state2) then
    if (counter = 64) then
        counter <= 0;
        dBit(to_integer(unsigned(index))) <= '0';
        sd_Offset <= 0;
        state_current <= state1;
        state <= "0001";
        stateRead <= "0001";
    else
        if (counter mod 2 = 1) then
            sd_MEMSTRB <= '0';
        else
            s_CS <= cpu_CS;
            sd_Addr(4 downto 0) <=
                STD_LOGIC_VECTOR(to_unsigned(sd_Offset, offset'length));
            sd_WRRD <= '1';
            s_Addr(7 downto 5) <= index;
            s_Addr(4 downto 0) <=
                STD_LOGIC_VECTOR(to_unsigned(sd_Offset, offset'length));
            s_Wen <= "0";
            sd_MEMSTRB <= '1';
            sd_Offset <= sd_Offset + 1;
        end if;
        counter <= counter + 1;
    end if;
State 3
elsif(state_current = state3) then
    cpu_Trig <= '1';
    state_current <= state4;
    state <= "0100";
    stateRead <= "0100";
end if;
end if;
d process;
-- Behavior --

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
entity SDRAM is
    Port (
        clk : in STD_LOGIC;
        ADDR : in STD_LOGIC_VECTOR (15 downto 0);
        WR_RD : in STD_LOGIC;
        MEMSTRB : in STD_LOGIC;
        DIN : in STD_LOGIC_VECTOR (7 downto 0);
        DOUT : out STD_LOGIC_VECTOR (7 downto 0)
    );
end SDRAM;
architecture Behavior of SDRAM is
    -- SDRAM Array
    type sdmemory is array (7 downto 0, 31 downto 0) of std_logic_vector(7 downto 0);
    signal sd_SIG: sdmemory;
    signal initialized : integer := 0;
begin
    process (clk)
    begin
        if (clk'event AND clk = '1') then
            if (initialized = 0) then
                for I in 0 to 7 loop
                    for J in 0 to 31 loop
                        sd_SIG(I,J) <= "11110000";
                    end loop;
                end loop;
                initialized <= 1;
            end if;
            if (MEMSTRB = '1') then
                if (WR_RD = '1') then
                    sd_SIG(to_integer(unsigned(ADDR(7 downto 5))),to_integer(unsigned(ADDR(4 downto 0)))) <= DIN;
                else
                    DOUT <= sd_SIG(to_integer(unsigned(ADDR(7 downto 5))),to_integer(unsigned(ADDR(4 downto 0))));
                end if;
            end if;
        end if;
    end process;
end Behavior;

```

```

-----
se IEEE.STD_LOGIC_1164.ALL;

entity topLevel is
  PORT(
    CLOCK : in std_logic;
    RESET : in std_logic;
    START : in std_logic;

    ADDR_CACHE, ADDR_SDRAM : out std_logic_vector(15 downto 0);
    ADDR_SRAM : out std_logic_vector(7 downto 0);
    DIN_CPU, DOUT_CPU, DIN_SDRAM, DOUT_SDRAM, DIN_SRAM, DOUT_SRAM : out std_logic_vector(7 downto 0);
    O_RDY, O_CS, WEN_CACHE, MUX_IN, MUX_OUT, WEN_SRAM, WEN_SDRAM, MEN_STRB : out std_logic;
    CPU_STATE : out std_logic_vector(3 downto 0)
  );
end topLevel;

architecture Behavioral of topLevel is
  --SRAM Component
  component SRAM
    Port (
      clk : in STD_LOGIC;
      wea : in STD_LOGIC_VECTOR(0 downto 0);
      addr : in STD_LOGIC_VECTOR(7 downto 0);
      dina : in STD_LOGIC_VECTOR(7 downto 0);
      douta : out STD_LOGIC_VECTOR(7 downto 0)
    );
  end component;

  --Cache Controller Component
  component CacheController
    Port (
      CLK : in STD_LOGIC;
      cpu_addr : in STD_LOGIC_VECTOR (15 downto 0);
      cpu_wea : in STD_LOGIC;
      cpu_cs : in STD_LOGIC;

      ad_addr : out STD_LOGIC_VECTOR (15 downto 0);
      ad_wea : out STD_LOGIC;
    );
  end component;

  s_addr : out std_logic_vector (15 downto 0);
  s_wen : out std_logic_vector(0 downto 0);
  s_cs : out std_logic;

  cpu_trig : out std_logic

);
end component;

--SDRAM Component
component sdram
  Port (CLK : in STD_LOGIC;
        ADDR : in STD_LOGIC_VECTOR (15 downto 0);
        WR_RD : in STD_LOGIC;
        MENSTRB : in STD_LOGIC;
        DIN : in STD_LOGIC_VECTOR (7 downto 0);
        DOUT : out STD_LOGIC_VECTOR (7 downto 0)
  );
end component;

--CPU Component
component CPU_gen
  Port (
    clk : in STD_LOGIC;
    rst : in STD_LOGIC;
    trig : in STD_LOGIC;
    Din : in STD_LOGIC_VECTOR (7 downto 0);
    Address : out STD_LOGIC_VECTOR (15 downto 0);
    wr_rd : out STD_LOGIC;
    cs : out STD_LOGIC;
    DOut : out STD_LOGIC_VECTOR (7 downto 0)
  );
end component;

signal addrCache, addrSDRAM : std_logic_vector(15 downto 0) := (others => '0');
signal addrSRAM : std_logic_vector(7 downto 0) := (others => '0');
signal dinCPU, doutCPU, dinSDRAM, doutSDRAM, dinSRAM, doutSRAM : std_logic_vector(7 downto 0) := (others => '0');
signal rdy, cs, wenCache, muxIn, muxOut, wenSRAM, menstrb : std_logic := '0';
signal trig : std_logic := '0';
signal wenSRAM : STD_LOGIC_VECTOR(0 downto 0);

```

```

--SRAM
SRAM_1: SRAM port map(
  clka => CLOCK,
  addra => addrSRAM,
  wea => wenSRAM,
  dina => dinSRAM,
  douta => doutSRAM
);

CacheController_1: CacheController port map(
  CLK => CLOCK,
  cpu_Addr => addrCache,
  cpu_WRED => wenCache,
  cpu_CS => cs,

  sd_Addr => addrSDRAM,
  sd_WRED => wenSDRAM,
  sd_MEMSTRB => memstrb,

  s_Addr => addrSRAM,
  s_Wen(0) => wenSRAM(0),
  s_CS => muxIn,

  cpu_Trig => rdy
);

adramC: adram port map(
  CLK => CLOCK,
  ADDR => addrSDRAM,
  WR_RD => wenSDRAM,
  MEMSTRB => memstrb,
  DIN => dinSDRAM,
  DOUT => doutSDRAM
);

CPU: CPU_gen port map(
  clk => CLOCK,
  rst => RESET,
  trig => trig,
  Din => dinCPU,

  Address => addrCache,
  wr_rd => wenCache,
  cs => cs,
  Dout => doutCPU
);

trigMax: process(START, rdy)
begin
  if(START = '1') then
    trig <= '1';
  else
    trig <= rdy;
  end if;
end process;

dataInputSRAM: process(muxIn, doutCPU, doutSRAM)
begin
  if(muxIn = '0') then
    dinSRAM <= doutCPU;
  else
    dinSRAM <= doutSDRAM;
  end if;
end process;

```

```

dataOutputSRAM: process(muxOut, doutSRAM)
begin
  if(muxOut = '0') then
    dinSDRAM <= doutSRAM;
  else
    dinCPU <= doutSRAM;
  end if;
end process;

debug: process(addrCache, addrSDRAM, addrSRAM, dinCPU, doutCPU, dinSDRAM, doutSDRAM,
  begin
    ADDR_CACHE <= addrCache;
    ADDR_SDRAM <= addrSDRAM;
    ADDR_SRAM <= addrSRAM;
    DIN_CPU <= dinCPU;
    DOUT_CPU <= doutCPU;
    DIN_SDRAM <= dinSDRAM;
    DOUT_SDRAM <= doutSDRAM;
    DIN_SRAM <= dinSRAM;
    DOUT_SRAM <= doutSRAM;
    O_RDY <= trig;
    O_CS <= cs;
    WEN_CACHE <= wenCache;

```

```

begin
  ADDR_CACHE <= addrCache;
  ADDR_SDRAM <= addrSDRAM;
  ADDR_SRAM <= addrSRAM;
  DIN_CPU <= dinCPU;
  DOUT_CPU <= doutCPU;
  DIN_SDRAM <= dinSDRAM;
  DOUT_SDRAM <= doutSDRAM;
  DIN_SRAM <= dinSRAM;
  DOUT_SRAM <= doutSRAM;
  O_RDY <= trig;
  O_CS <= cs;
  WEN_CACHE <= wenCache;
  MUX_IN <= muxIn;
  MUX_OUT <= muxOut;
  WEN_SRAM <= wenSRAM(0);
  WEN_SDRAM <= wenSDRAM;
  MEM_STRB <= memstrb;
end process;
i Behavioral;

```



```

COMPONENT CPU_gen
PORT(
    clk : IN std_logic;
    rst : IN std_logic;
    trig : IN std_logic;
    Address : OUT std_logic_vector(15 downto 0);
    wr_rd : OUT std_logic;
    cs : OUT std_logic;
    DOut : OUT std_logic_vector(7 downto 0)
);
END COMPONENT;

```

```

Inst_CPU_gen: CPU_gen PORT MAP(
    clk => ,
    rst => ,
    trig => ,
    Address => ,
    wr_rd => ,
    cs => ,
    DOut =>
);

```

```

Port ( clk : in STD_LOGIC;
        WR_RD : in STD_LOGIC;
        CS : in STD_LOGIC;
        CPU_ADD : in STD_LOGIC_VECTOR (15 downto 0);
        SDRAM_ADD : out STD_LOGIC_VECTOR(15 DOWNT0 0);
        CACHE_ADD : out STD_LOGIC_VECTOR(7 DOWNT0 0);

        CACHE_WEN : out STD_LOGIC;
        CACHE_DIN_WEN : out STD_LOGIC;
        CACHE_DOUT_WEN : out STD_LOGIC;
        WEN_SDRAM : out STD_LOGIC;
        MEMSTRB : out STD_LOGIC;
        RDY : out STD_LOGIC;
        DEBUG : out STD_LOGIC_VECTOR(31 DOWNT0 0));
end CacheControllerFSM;

architecture Behavioral of CacheControllerFSM is
    -- Array of 8 blocks of dirty and valid bits
    type dirty_bits is array (7 downto 0) of STD_LOGIC;
    signal dbits: dirty_bits := (others => '0');
    type valid_bits is array (7 downto 0) of STD_LOGIC;
    signal vbits: valid_bits := (others => '0');
    -- CPU signals
    signal cpu_tag : STD_LOGIC_VECTOR(7 DOWNT0 0);
    signal cpu_index : STD_LOGIC_VECTOR(2 DOWNT0 0);
    signal cpu_offset : STD_LOGIC_VECTOR(4 DOWNT0 0);
    signal index_and_offset : STD_LOGIC_VECTOR(7 DOWNT0 0);
    -- Tag compare component
    COMPONENT TagCompareDirectMapping
    PORT(
        CPU_ADD : IN std_logic_vector(15 downto 0);
        -- ...
    );

```

```

PORT(
    CPU_ADD : IN std_logic_vector(15 downto 0);
    clk : IN std_logic;
    HIT_MISS : OUT std_logic
);
END COMPONENT;

begin
    -- Continuous assignment of CPU signals
    cpu_tag <= CPU_ADD(15 DOWNTO 8);
    cpu_index <= CPU_ADD(7 DOWNTO 5);
    cpu_offset <= CPU_ADD(4 DOWNTO 0);
    index_and_offset <= CPU_ADD(7 DOWNTO 0);
    sys_tag_compare: TagCompareDirectMapping PORT MAP(
        CPU_ADD => CPU_ADD,
        clk => clk,
        HIT_MISS => hit_miss_signal
    );

```

```

begin
    if(clk'Event AND clk='1') then
        case yfsm is
            -- Processing s0 - Idle
            when s0 =>
                if(CS = '1') then
                    yfsm <= s1;
                    DEBUG(2 DOWNTO 0) <= "001";
                end if;
            --

```

```

when s1 =>
    if(hit_miss_signal='1' AND WR_RD='1') then
        yfsm <= s2;
        DEBUG(2 DOWNTO 0) <= "010";
    elsif(hit_miss_signal='1' AND WR_RD='0') then
        yfsm <= s3;
        DEBUG(2 DOWNTO 0) <= "011";
    elsif(hit_miss_signal='0' AND dbits(to_integer(unsigned(cpu_index)))='0') then
        yfsm <= s4;
        DEBUG(2 DOWNTO 0) <= "100";
    elsif(hit_miss_signal='0' AND dbits(to_integer(unsigned(cpu_index)))='1') then
        yfsm <= s5;
        DEBUG(2 DOWNTO 0) <= "101";
    end if;
    -- Processing s2 - Cache hit and write
    when s2 =>
        -- if(cpu_rdy='1') then

```

```

        DEBUG(2 DOWNTO 0) <= "000";
-- Processing s3 - Cache hit and read
when s3 =>
    -- if(cpu_rdy='1') then
    --     yfsm <= s0;
    -- else
    --     yfsm <= s3;
    -- end if;
    yfsm <= s0;
    DEBUG(2 DOWNTO 0) <= "000";
-- Processing s4 - Cache miss and dirty bit=0
when s4 =>
    if(WR_RD='0') then
        yfsm <= s3;
        DEBUG(2 DOWNTO 0) <= "011";
    elsif(WR_RD='1') then
        yfsm <= s2;
        DEBUG(2 DOWNTO 0) <= "010";
    -- elsif(menstrb='0') then
    --     yfsm <= s4;
    end if;

```

```

when s4 =>
    if(WR_RD='0') then
        yfsm <= s3;
        DEBUG(2 DOWNTO 0) <= "011";
    elsif(WR_RD='1') then
        yfsm <= s2;
        DEBUG(2 DOWNTO 0) <= "010";
    -- elsif(menstrb='0') then
    --     yfsm <= s4;
    end if;
-- Processing s5 - Cache miss and dirty bit=1
when s5 =>
    -- if(menstrb='1') then
    --     yfsm <= s4;
    -- else
    --     yfsm <= s5;
    -- end if;
    yfsm <= s4;
    DEBUG(2 DOWNTO 0) <= "100";

```

```

-- -- --
end process;
process(yfsm)
begin
    case yfsm is
        -- Generating outputs for s0
        when s0 =>
            RDY <= '1';
        -- Generating outputs for s1
        when s1 =>
            RDY <= '0';
        -- Generating outputs for s2
        when s2 =>
            CACHE_ADD <= index_and_offset;
            CACHE_WEN <= '1';
            CACHE_DIN_WEN <= '0';
            dbits(to_integer(unsigned(cpu_index))) <= '1'; --dirty bit
            vbits(to_integer(unsigned(cpu_index))) <= '1'; --valid bit
            -- RDY <= '1'; -- This should happen when going back to s0
        -- Generating outputs for s3
        when s3 =>
            CACHE_ADD <= index_and_offset;
            CACHE_WEN <= '0';
            CACHE_DOUT_WEN <= '1';
            -- RDY <= '1'; -- This should happen when going back to s0
        -- Generating outputs for s4
        when s4 =>
            SDRAM_ADD <= (cpu_add AND "111111111100000");
            WEN_SDRAM <= '0';
            CACHE_DIN_WEN <= '1';
    end case;
end process;

```

```

        SDRAM_ADD <= (cpu_add AND "111111111100000");
        WEN_SDRAM <= '0';
        CACHE_DIN_WEN <= '1';
        CACHE_WEN <= '1';
        vbits(to_integer(unsigned(cpu_index))) <= '1';
        -- Generating outputs for s5
        when s5 =>
            SDRAM_ADD <= (cpu_add AND "111111111100000");
            WEN_SDRAM <= '1';
            CACHE_DOUT_WEN <= '0';
            MEMSTRB <= '1';
    end case;
end process;

DEBUG(3) <= dbits(to_integer(unsigned(cpu_index)));
DEBUG(4) <= vbits(to_integer(unsigned(cpu_index)));

```

end Behavioral;